

## Homework #1

Due date : Mar. 20<sup>th</sup>, 2025

Please submit your **report (\*.pdf)** and **netlist file (\*.sp)** to the EECLASS system.

Please name your file as *hw1\_student number.pdf*, *hw1\_student number\_x.sp*

e.g. hw1\_100061501\_1c.sp represents .sp file for question 1(c).

Note:

Don't use black color in background for your screen capture figures.

List calculation/design process clearly and mark proper information of all plots/figures required.

## (1) Above-threshold Device parameters and Amplifier Design

Consider the amplifier in Fig.1 with  $C_L=1\text{pF}$  and  $V_{DD}=1.8\text{V}$ . Please design the transistor sizes,  $(W/L)_i$ , to achieve a small-signal gain of  $A_V \equiv v_o/v_i > 60(V/V)$ ,  $f_{3dB} > 650\text{kHz}$ ,  $\text{Power} \leq 250\mu\text{W}$

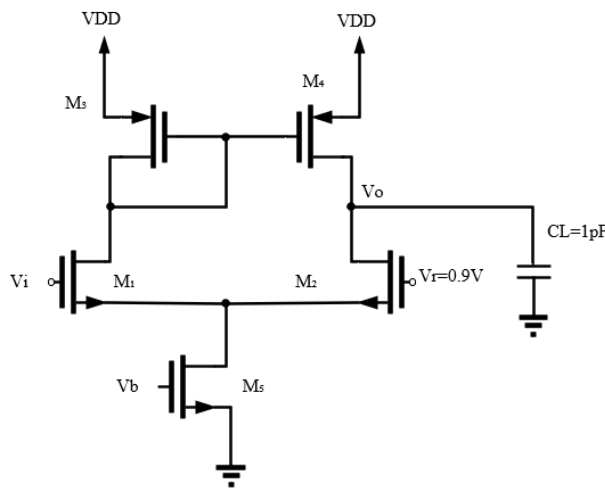


Fig.1

- Estimate the values of the Level-1 parameters** in Table.1-1 for both NMOS & PMOS transistors according to the equations in Table.1-1 and parameter values in your Spice file (\*.l). Please give the units for the parameters in your report.  
(Hint : Select one N\_18.x and one P\_18.x (e.g. N\_18.1) models, which you may use in your design, from the Spice file.)
- Use the Level-1 parameters obtained in (a) to design  $(W/L)_i$  **by hand calculation**.  
(Hint : You could start from determining a biasing current which you think is proper, and then check whether  $f_{3dB}$  and  $A_V$  are satisfied)
- With  $(W/L)_i$  set to the values designed in (b), Use **Virtuoso Spectre** to (i) calculate the operating modes,  $g_m$ ,  $r_o$  of all transistors when  $v_I = v_{REF} = 0.9\text{V}$ . Give the **summary of circuit operations** in your report. (ii) sweep the DC value of  $v_O$  with  $v_I$  sweeping from 0 to VDD. Give the **plot of  $v_O$  v.s.  $v_I$**  in your report, and **mark maximum gain value** on the plot. (iii) sweep the frequency response of  $v_O/v_I$  as  $v_I = v_{REF} = 0.9\text{V}$ . Give the **plot of the frequency response**.
- Compare the differences** between simulation results and hand calculation, and **discuss which Level-1 parameters estimated in (a)** is imprecise, and thus causing these differences.) **Re-estimate these Level-1 parameters** that you think imprecise by sweeping the  $I_d$ - $V_{gs}$  or  $I_d$ - $V_{ds}$  of individual transistors in Spectre and then extracting parameters values from the simulated I-V curves.

- e) Use re-estimated Level-1 parameters to design  $(W/L)_i$  by **hand calculation**.
- f) Use Spectre to simulate the design in (e). Give **summary of circuit operations, the plot of  $v_O$  v.s.  $v_I$ , and the frequency response** in your report. If necessary, repeat step (e)-(f) to **tune** the  $(W/L)_i$  to meet  $A_V > 60$ ,  $f_{3dB} > 650kHz$ , and the **DC biasing conditions** you designed. **Please explain all the adjustments you made.**

Parameter	Equation	Unit
$V_{TH0}$	$V_{TH0}$	V
K	$\mu_0 C_{ox}$ where $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$	$\mu A/V^2$
$\lambda$	Use 0.02 for NMOS and 0.04 for PMOS	
$\gamma$	$\frac{\sqrt{2\epsilon_{si}qN_{SUB}}}{C_{ox}}$	$V^{1/2}$
$2 \phi_F $	$2 \frac{kT}{q} \ln\left(\frac{N_{SUB}}{n_i}\right)$	V

Note :  $N_{SUB}$  correspond to “nch” in the Spice model we use

**Tabel.1-1: Level 1 parameters of a MOS transistor**

Constant Symbol	Constant Description	Value	Units
$V_G$	Silicon bandgap (27°C)	1.205	V
$k$	Boltzmann's constant	$1.381 \times 10^{-23}$	J/K
$n_i$	Intrinsic carrier concentration (27°C)	$1.45 \times 10^{10}$	$cm^{-3}$
$\epsilon_0$	Permittivity of free space	$8.854 \times 10^{-14}$	F/cm
$\epsilon_{Si}$	Permittivity of silicon	$11.7 \epsilon_0$	F/cm
$\epsilon_{ox}$	Permittivity of SiO <sub>2</sub>	$3.9 \epsilon_0$	F/cm

**Table.1-2: Silicon constants**

## (2) Subthreshold Device parameters and Amplifier Design

Consider the differential amplifier in Fig.2 with  $C_L=1pF$  and  $V_{DD}=1V$ . Please follow the steps below to **design** the sizes of all transistors to satisfy the specifications in Table.2-1

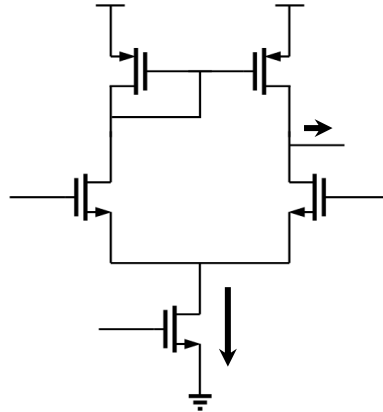


Fig.2

	Specifications	Units
DC characteristics	$Max. P_{diss} \leq 500 (V_{DD} = 1V)$	nW
AC characteristics	$A_v \geq 60$	V/V
	$f_{3dB} \geq 10k$	Hz
Transient characteristic	Slew rate $\geq 0.3$	V/ $\mu s$

Table.2-1

- Choose a size (W/L) for a PMOS and an NMOS transistors. Use Spectre to simulate and plot the  $I_D$ - $V_{GS}$  curves of the selected NMOS and PMOS operating in the **subthreshold region**. According to the model (equation) of  $I_D$ - $V_{GS}$  in subthreshold operation, **extract the parameters  $I_{s0}$  and  $\kappa$**  from the simulated curves. In your report, please show the Spectre-simulated  $I_D$ - $V_{GS}$  curves and describe clearly how the parameters are derived. Afterwards, please **plot a figure that compares** (a) the  $I_D$ - $V_{GS}$  curve simulated by Spectre with (b) the  $I_D$ - $V_{GS}$  curve generated according to the equation with the extracted  $I_{s0}$  and  $\kappa$ .
- Describe clearly how you **select the biasing current and voltage**, as well as how you **calculate all transistor sizes** in your design.
- Use **DC analysis** in Spectre to simulate  $I_{out}$  versus  $(V^+ - V^-)$  as  $V^- = 0.5V$  and  $V^+$  sweeps from 0 to 1V. Does  $I_{out}$  agree with your derivation in the question (b)? Is the **power dissipation** smaller than 500nW? If not, please adjust the transistor sizes, explain the adjustments you made, and show the simulated result of the new design in your report.
- Use **AC analysis** to simulate the frequency response of the amplifier and show the result in your report. Is the specification of **AC characteristics** achieved? If not, please adjust the transistor sizes, explain the adjustments you made, and show the simulated result of the new design in your report.
- Connect the amplifier as a unit-gain buffer. Use **transient analysis** to apply a step input from 0.25 to 0.75 V and plot the corresponding transient response of  $V_{out}$  in your report. Is the **slew rate** achieved? If not, please adjust the transistor sizes, explain the adjustments you made, and show the simulated result of the new design in your report.